

1. Given a 4-variable logic expression, simplify it using appropriate technique and simulate the same using basic gates

Code

```
module four_var_logic (
    input A,
    input B,
    input C,
    input D,
    output Y
);
    assign Y = (C & D) | (~A & D); // Y = CD + A'D
endmodule
```

TestBench

```
`timescale 1ns / 1ps
module testbench;
    reg A, B, C, D;
    wire Y;
    four_var_logic uut (
        .A(A),
        .B(B),
        .C(C),
        .D(D),
        .Y(Y)
    );

    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(1);
        $monitor("A=%b, B=%b, C=%b, D=%b, Y=%b", A, B, C, D, Y);
        A = 0; B = 0; C = 0; D = 0; #10;
        A = 0; B = 0; C = 1; D = 0; #10;
        A = 1; B = 0; C = 1; D = 1; #10;
        A = 1; B = 1; C = 0; D = 1; #10;
        A = 1; B = 1; C = 1; D = 1; #10;
        $finish;
    end

endmodule
```

Output



2. Design a 4 bit full adder and subtractor and simulate the same using basic gates.

Code for Adder

```
module FullAdder4bit (  
    input [3:0] A,  
    input [3:0] B,  
    input Cin,  
    output [3:0] Sum,  
    output Cout  
);  
    wire C1, C2, C3;  
    // 1st bit  
    FullAdder FA1(A[0], B[0], Cin, Sum[0], C1);  
    // 2nd bit  
    FullAdder FA2(A[1], B[1], C1, Sum[1], C2);  
    // 3rd bit  
    FullAdder FA3(A[2], B[2], C2, Sum[2], C3);  
    // 4th bit  
    FullAdder FA4(A[3], B[3], C3, Sum[3], Cout);  
endmodule
```

```
module FullAdder (  
    input A,  
    input B,  
    input Cin,  
    output Sum,  
    output Cout  
);  
    assign Sum = A ^ B ^ Cin;  
    assign Cout = (A & B) | (A & Cin) | (B & Cin);  
endmodule
```

TestBench

```
module testbench;  
    reg [3:0] A, B;  
    reg Cin;  
    wire [3:0] Sum;  
    wire Cout;  
    FullAdder4bit uut (  
        .A(A),  
        .B(B),  
        .Cin(Cin),  
        .Sum(Sum),  
        .Cout(Cout)  
    );  
endmodule
```

```

initial begin
  $dumpfile("dump.vcd");
  $dumpvars(1);
  $monitor("A=%b, B=%b, Cin=%b, Sum=%b, Cout=%b", A, B, Cin, Sum, Cout);


  A = 4'b0000; B = 4'b0000; Cin = 0; #10;
  A = 4'b0001; B = 4'b0001; Cin = 0; #10;
  A = 4'b0010; B = 4'b0010; Cin = 0; #10;
  A = 4'b0011; B = 4'b0011; Cin = 0; #10;
  A = 4'b1111; B = 4'b1111; Cin = 0; #10;

  $finish;
end

endmodule

```

Output:

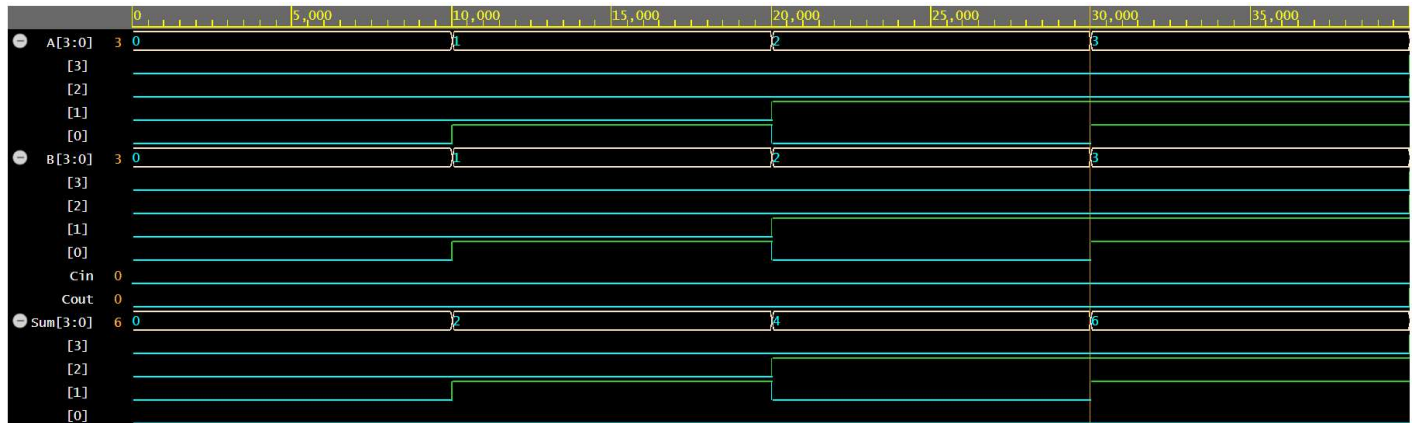

Code for Subtractor

```
module FullSubtractor4bit (  
    input [3:0] A,  
    input [3:0] B,  
    input Bin,  
    output [3:0] Diff,  
    output Bout  
);  
    wire B1, B2, B3;  
    // 1st bit  
    FullSubtractor FS1(A[0], B[0], Bin, Diff[0], B1);  
    // 2nd bit  
    FullSubtractor FS2(A[1], B[1], B1, Diff[1], B2);  
    // 3rd bit  
    FullSubtractor FS3(A[2], B[2], B2, Diff[2], B3);  
    // 4th bit  
    FullSubtractor FS4(A[3], B[3], B3, Diff[3], Bout);  
endmodule  
  
module FullSubtractor (  
    input A,  
    input B,  
    input Bin,  
    output Diff,  
    output Bout  
);  
    assign Diff = A ^ B ^ Bin;  
    assign Bout = (~A & B & Bin) | (A & ~B & Bin);  
endmodule
```

TestBench


```
module testbench;  
    reg [3:0] A, B;  
    reg Bin;  
    wire [3:0] Diff;  
    wire Bout;  
  
    FullSubtractor4bit uut (  
        .A(A),  
        .B(B),  
        .Bin(Bin),  
        .Diff(Diff),  
        .Bout(Bout)  
    );  
endmodule
```

```

initial begin
  $dumpfile("dump.vcd");
  $dumpvars(1);
  $monitor("A=%b, B=%b, Bin=%b, Diff=%b, Bout=%b", A, B, Bin, Diff, Bout);
  A = 4'b0000; B = 4'b0000; Bin = 0; #10;
  A = 4'b0001; B = 4'b0001; Bin = 0; #10;
  A = 4'b0010; B = 4'b0010; Bin = 0; #10;
  A = 4'b0011; B = 4'b0011; Bin = 0; #10;
  A = 4'b1111; B = 4'b1111; Bin = 0; #10;
  $finish;
end
endmodule

```

Output

 

3. Design Verilog HDL to implement simple circuits using structural, Data flow and Behavioural model.

Code

TestBench

Output

4. Design Verilog HDL to implement Binary Adder-Subtractor – Half and Full Adder, Half and Full Subtractor.

Code

```
module half_adder(
    input A,
    input B,
    output sum,
    output carry
);
    assign sum = A ^ B;
    assign carry = A & B;
endmodule

module full_adder(
    input A,
    input B,
    input Cin,
    output sum,
    output Cout
);
    wire sum1, carry1, carry2;
    half_adder HA1(A, B, sum1, carry1);
    half_adder HA2(sum1, Cin, sum, carry2);
    assign Cout = carry1 | carry2;
endmodule

module half_subtractor(
    input A,
    input B,
    output difference,
    output borrow
);
    assign difference = A ^ B;
    assign borrow = (~A & B);
endmodule

module full_subtractor(
    input A,
    input B,
    input Bin,
    output difference,
    output Bout
);
    wire diff1, bor1, bor2;
    half_subtractor HS1(A, B, diff1, bor1);
```



```

half_subtractor HS2(diff1, Bin, difference, bor2);
assign Bout = bor1 | bor2;
endmodule

```

```

module binary_adder_subtractor(
    input [3:0] A,
    input [3:0] B,
    input SUB,
    output [3:0] result,
    output overflow
);
    wire [3:0] sum;
    wire [3:0] difference;
    wire carry_in, borrow_in, carry_out, borrow_out;
    assign carry_in = ~SUB;
    assign borrow_in = SUB;
    full_adder FA0(A[0], B[0], carry_in, sum[0], carry_out);
    full_adder FA1(A[1], B[1], carry_out, sum[1], carry_out);
    full_adder FA2(A[2], B[2], carry_out, sum[2], carry_out);
    full_adder FA3(A[3], B[3], carry_out, sum[3], carry_out);
    full_subtractor FS0(A[0], B[0], borrow_in, difference[0], borrow_out);
    full_subtractor FS1(A[1], B[1], borrow_out, difference[1], borrow_out);
    full_subtractor FS2(A[2], B[2], borrow_out, difference[2], borrow_out);
    full_subtractor FS3(A[3], B[3], borrow_out, difference[3], borrow_out);
    assign result = (SUB) ? difference : sum;
    assign overflow = carry_out ^ borrow_out;
endmodule

```

TestBench

```

module testbench;
    reg [3:0] A, B;
    reg SUB;
    wire [3:0] result;
    wire overflow;
    binary_adder_subtractor DUT (
        .A(A),
        .B(B),
        .SUB(SUB),
        .result(result),
        .overflow(overflow)
    );
    initial begin
        $dumpfile("dump.vcd");
    end
endmodule


```

```

$dumpvars(1);
$monitor("Time=%0t, A=%b, B=%b, SUB=%b, result=%b, overflow=%b", $time, A, B, SUB, result,
overflow);
A = 4'b0101; B = 4'b0011; SUB = 0; #10;
A = 4'b0101; B = 4'b0011; SUB = 1; #10;
A = 4'b1111; B = 4'b0001; SUB = 0; #10;
A = 4'b0000; B = 4'b0001; SUB = 1; #10;
A = 4'b0101; B = 4'b0011; SUB = 0; #10;
end
endmodule

```

Output

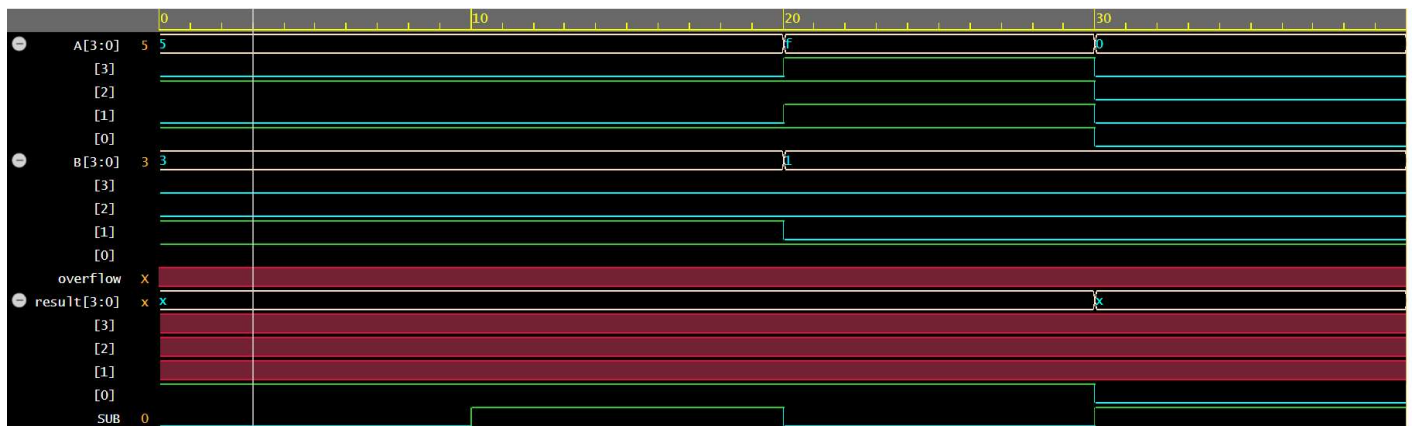

5. Design Verilog HDL to implement Decimal adder.

Code:

```
module DecimalAdder(
    input [3:0] A,
    input [3:0] B,
    output reg [3:0] Sum
);

    reg [3:0] A_binary;
    reg [3:0] B_binary;
    reg [4:0] binary_sum;

    always @* begin
        case(A)
            0: A_binary = 4'b0000;
            1: A_binary = 4'b0001;
            2: A_binary = 4'b0010;
            3: A_binary = 4'b0011;
            4: A_binary = 4'b0100;
            5: A_binary = 4'b0101;
            6: A_binary = 4'b0110;
            7: A_binary = 4'b0111;
            8: A_binary = 4'b1000;
            9: A_binary = 4'b1001;
            default: A_binary = 4'b0000;
        endcase

        case(B)
            0: B_binary = 4'b0000;
            1: B_binary = 4'b0001;
            2: B_binary = 4'b0010;
            3: B_binary = 4'b0011;
            4: B_binary = 4'b0100;
            5: B_binary = 4'b0101;
            6: B_binary = 4'b0110;
            7: B_binary = 4'b0111;
            8: B_binary = 4'b1000;
            9: B_binary = 4'b1001;
            default: B_binary = 4'b0000;
        endcase
    end

    always @* begin
```

```

    binary_sum = A_binary + B_binary;
end

always @* begin
    case(binary_sum)
        0: Sum = 4'b0000;
        1: Sum = 4'b0001;
        2: Sum = 4'b0010;
        3: Sum = 4'b0011;
        4: Sum = 4'b0100;
        5: Sum = 4'b0101;
        6: Sum = 4'b0110;
        7: Sum = 4'b0111;
        8: Sum = 4'b1000;
        9: Sum = 4'b1001;
        10: Sum = 4'b0000;
        11: Sum = 4'b0000;
        12: Sum = 4'b0000;
        13: Sum = 4'b0000;
        14: Sum = 4'b0000;
        15: Sum = 4'b0000;
        default: Sum = 4'b0000;
    endcase
end
endmodule

```

TestBench:

```

module testbench();
    reg [3:0] A;
    reg [3:0] B;
    wire [3:0] Sum;
    DecimalAdder decimal_adder(
        .A(A),
        .B(B),
        .Sum(Sum)
    );

    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(1);
        $monitor("Time=%0t A=%d B=%d Sum=%d", $time, A, B, Sum);
        A = 0; B = 0; #10;
        A = 1; B = 2; #10;
        A = 3; B = 4; #10;
    end
endmodule


```

```

    A = 5; B = 6; #10;
    A = 7; B = 8; #10;
    $finish;
end
endmodule

```

Output:

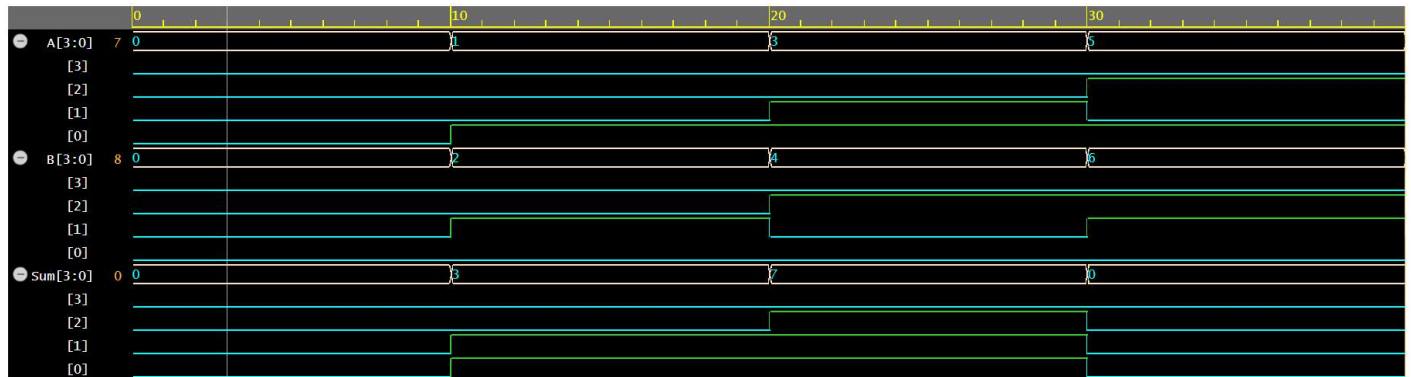

6. Design Verilog program to implement Different types of multiplexer like 2:1, 4:1 and 8:1.


Code for 2:1:

```
module mux2to1(  
    input a,  
    input b,  
    input sel,  
    output y  
);  
    assign y = (sel) ? b : a;  
endmodule
```

TestBench:

```
module testbench;  
    reg a, b, sel;  
    wire y;  
    mux2to1 DUT (  
        .a(a),  
        .b(b),  
        .sel(sel),  
        .y(y)  
    );  
  
    initial begin  
        $dumpfile("dump.vcd");  
        $dumpvars(1);  
        $monitor("Time=%0t, a=%b, b=%b, sel=%b, y=%b", $time, a, b, sel, y);  
        sel = 0; a = 1; b = 0; #10;  
        sel = 1; a = 0; b = 1; #10;  
        sel = 0; a = 0; b = 0; #10;  
        sel = 1; a = 1; b = 1; #10;  
        sel = 0; a = 1; b = 1; #10;  
    end  
endmodule
```

Output:

 


Code for 4:1:

```
module mux4to1(
input d0,
input d1,
input d2,
input d3,
input sel1,
input sel0,
output y
);
assign y = (sel1 == 1'b1) ? ((sel0 == 1'b1) ? d3 : d1) : ((sel0 == 1'b1) ? d2 : d0);
endmodule
```

Testbench:

```
module testbench;
reg d0, d1, d2, d3, sel1, sel0;
wire y;
mux4to1 DUT (
.d0(d0),
.d1(d1),
.d2(d2),
.d3(d3),
.sel1(sel1),
.sel0(sel0),
.y(y)
);
initial begin
$dumpfile("dump.vcd");
$dumpvars(1);
$monitor("Time=%0t, d0=%b, d1=%b, d2=%b, d3=%b, sel1=%b, sel0=%b, y=%b", $time, d0, d1, d2, d3,
sel1, sel0, y);
sel1 = 0; sel0 = 0; d0 = 0; d1 = 1; d2 = 0; d3 = 0; #10;
sel1 = 0; sel0 = 1; d0 = 0; d1 = 0; d2 = 1; d3 = 0; #10;
sel1 = 1; sel0 = 0; d0 = 1; d1 = 0; d2 = 0; d3 = 0; #10;
sel1 = 1; sel0 = 1; d0 = 0; d1 = 0; d2 = 0; d3 = 1; #10;
sel1 = 1; sel0 = 1; d0 = 1; d1 = 0; d2 = 1; d3 = 0; #10;
end
endmodule
```

Output:

 

Code for 8:1:

```
module mux8to1(
    input d0,
    input d1,
    input d2,
    input d3,
    input d4,
    input d5,
    input d6,
    input d7,
    input sel2,
    input sel1,
    input sel0,
    output y
);
    assign y = (sel2 == 1'b1) ? ((sel1 == 1'b1) ? ((sel0 == 1'b1) ? d7 : d5) : ((sel0 == 1'b1) ? d6 : d4)) : ((sel1 == 1'b1) ? ((sel0 == 1'b1) ? d3 : d1) : ((sel0 == 1'b1) ? d2 : d0));
endmodule
```

TestBench:

```
module testbench;
    reg d0, d1, d2, d3, d4, d5, d6, d7, sel2, sel1, sel0;
    wire y;
    mux8to1 DUT (
        .d0(d0),
        .d1(d1),
        .d2(d2),
        .d3(d3),
        .d4(d4),
        .d5(d5),
        .d6(d6),
        .d7(d7),
        .sel2(sel2),
        .sel1(sel1),
        .sel0(sel0),
        .y(y)
    );
endmodule
```



```


);

initial begin
  $dumpfile("dump.vcd");
  $dumpvars(1);
  $monitor("Time=%0t, d0=%b, d1=%b, d2=%b, d3=%b, d4=%b, d5=%b, d6=%b, d7=%b, sel2=%b, sel1=%b,
sel0=%b, y=%b", $time, d0, d1, d2, d3, d4, d5, d6, d7, sel2, sel1, sel0, y);
  sel2 = 0; sel1 = 0; sel0 = 0; d0 = 1; d1 = 0; d2 = 0; d3 = 0; d4 = 0; d5 = 0; d6 = 0; d7 = 0; #10;
  sel2 = 0; sel1 = 0; sel0 = 1; d0 = 0; d1 = 1; d2 = 0; d3 = 0; d4 = 0; d5 = 0; d6 = 0; d7 = 0; #10;
  sel2 = 0; sel1 = 1; sel0 = 0; d0 = 0; d1 = 0; d2 = 1; d3 = 0; d4 = 0; d5 = 0; d6 = 0; d7 = 0; #10;
  sel2 = 0; sel1 = 1; sel0 = 1; d0 = 0; d1 = 0; d2 = 0; d3 = 1; d4 = 0; d5 = 0; d6 = 0; d7 = 0; #10;
  sel2 = 1; sel1 = 0; sel0 = 0; d0 = 0; d1 = 0; d2 = 0; d3 = 0; d4 = 1; d5 = 0; d6 = 0; d7 = 0; #10;
  sel2 = 1; sel1 = 0; sel0 = 1; d0 = 0; d1 = 0; d2 = 0; d3 = 0; d4 = 0; d5 = 1; d6 = 0; d7 = 0; #10;
  sel2 = 1; sel1 = 1; sel0 = 0; d0 = 0; d1 = 0; d2 = 0; d3 = 0; d4 = 0; d5 = 0; d6 = 1; d7 = 0; #10;
  sel2 = 1; sel1 = 1; sel0 = 1; d0 = 0; d1 = 0; d2 = 0; d3 = 0; d4 = 0; d5 = 0; d6 = 0; d7 = 1; #10;
end

endmodule

```

Output:

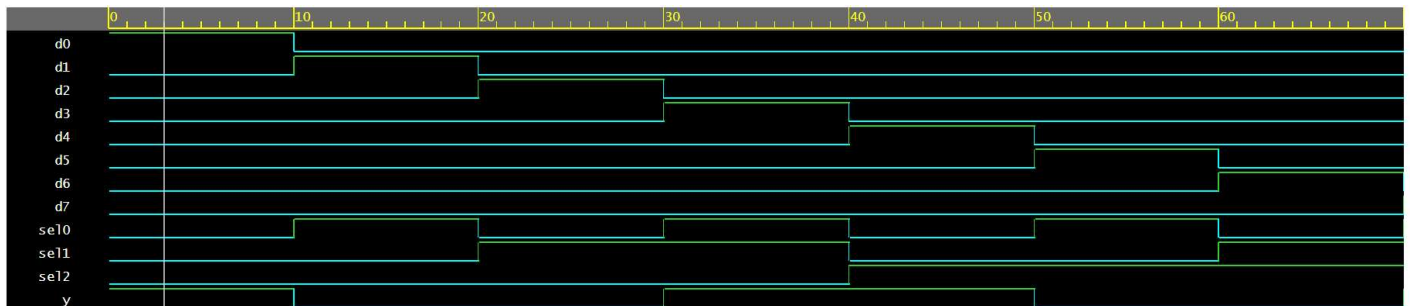

7. Design Verilog program to implement types of De-Multiplexer.

Code 1:2:

```
module demux1to2(  
    input d,  
    input sel,  
    output y0,  
    output y1  
);  
    assign y0 = ~sel & d;  
    assign y1 = sel & d;  
endmodule
```

TestBench:

```
module testbench;  
    reg d, sel;  
    wire y0, y1;  
    demux1to2 DUT (  
        .d(d),  
        .sel(sel),  
        .y0(y0),  
        .y1(y1)  
    );  
    initial begin  
        $dumpfile("dump.vcd");  
        $dumpvars(1);  
        $monitor("Time=%0t, d=%b, sel=%b, y0=%b, y1=%b", $time, d, sel, y0, y1);  
        sel = 0; d = 1; #10;  
        sel = 1; d = 0; #10;  
        sel = 0; d = 0; #10;  
        sel = 1; d = 1; #10;  
        sel = 1; d = 0; #10;  
    end  
endmodule
```

Output:




Code 1:4:

```
module demux2to4(  
    input d0,  
    input d1,  
    output y0,  
    output y1,  
    output y2,  
    output y3  
);  
    assign y0 = ~d1 & ~d0;  
    assign y1 = ~d1 & d0;  
    assign y2 = d1 & ~d0;  
    assign y3 = d1 & d0;  
endmodule
```

TestBench:

```
module testbench;  
    reg d0, d1;  
    wire y0, y1, y2, y3;  
    demux2to4 DUT (  
        .d0(d0),  
        .d1(d1),  
        .y0(y0),  
        .y1(y1),  
        .y2(y2),  
        .y3(y3)  
    );  
    initial begin  
        $dumpfile("dump.vcd");  
        $dumpvars(1);  
        $monitor("Time=%0t, d0=%b, d1=%b, y0=%b, y1=%b, y2=%b, y3=%b", $time, d0, d1, y0, y1, y2, y3);  
        d0 = 0; d1 = 0; #10;  
        d0 = 1; d1 = 0; #10;  
        d0 = 0; d1 = 1; #10;  
        d0 = 1; d1 = 1; #10;  
        d0 = 0; d1 = 1; #10;  
    end  
endmodule
```

Output:

 

Code 1:8:

```
module demux3to8(  
    input d0,  
    input d1,  
    input d2,  
    output y0,  
    output y1,  
    output y2,  
    output y3,  
    output y4,  
    output y5,  
    output y6,  
    output y7  
);  
    assign y0 = ~d2 & ~d1 & ~d0;  
    assign y1 = ~d2 & ~d1 & d0;  
    assign y2 = ~d2 & d1 & ~d0;  
    assign y3 = ~d2 & d1 & d0;  
    assign y4 = d2 & ~d1 & ~d0;  
    assign y5 = d2 & ~d1 & d0;  
    assign y6 = d2 & d1 & ~d0;  
    assign y7 = d2 & d1 & d0;  
endmodule
```

TestBench:

```
module testbench;  
    reg d0, d1, d2;  
    wire y0, y1, y2, y3, y4, y5, y6, y7;  
    demux3to8 DUT (  
        .d0(d0),  
        .d1(d1),  
        .d2(d2),  
        .y0(y0),  
        .y1(y1),  
        .y2(y2),  
        .y3(y3),  
        .y4(y4),
```

```

.y5(y5),
.y6(y6),
.y7(y7)
);

initial begin
  $dumpfile("dump.vcd");
  $dumpvars(1);
  $monitor("Time=%0t, d0=%b, d1=%b, d2=%b, y0=%b, y1=%b, y2=%b, y3=%b, y4=%b, y5=%b, y6=%b,
y7=%b", $time, d0, d1, d2, y0, y1, y2, y3, y4, y5, y6, y7);
  d0 = 0; d1 = 0; d2 = 0; #10;
  d0 = 1; d1 = 0; d2 = 0; #10;
  d0 = 0; d1 = 1; d2 = 0; #10;
  d0 = 1; d1 = 1; d2 = 0; #10;
  d0 = 0; d1 = 0; d2 = 1; #10;
end
endmodule

```

Output:



8. Design Verilog program for implementing various types of Flip-Flops such as SR, JK and D.

Code:

```
module sr_ff(  
    input clk,  
    input S,  
    input R,  
    output reg Q  
);  
always @(posedge clk) begin  
    if (S && ~R) begin  
        Q<=1'b1;  
    end  
    else if (~S && R) begin  
        Q<=1'b0;  
    end  
end  
endmodule
```

TestBench:

```
module testbench;  
    reg clk, S, R;  
    wire Q;  
    sr_ff DUT (  
        .clk(clk),  
        .S(S),  
        .R(R),  
        .Q(Q)  
    );  
    always #5 clk = ~clk;  
    initial begin  
        $dumpfile("dump.vcd");  
        $dumpvars(1);  
        $monitor("Time=%0t, clk=%b, S=%b, R=%b, Q=%b", $time, clk, S, R, Q);  
        S = 0; R = 0; #10;  
        S = 1; R = 0; #10;  
        S = 0; R = 1; #10;  
        S = 1; R = 1; #10;  
        S = 0; R = 1; #10;  
        $finish;  
    end  
endmodule
```

Output:

